

Chapter 3

Arithmetic for Computers




Arithmetic for Computers

- Operations on integers
 - Addition and subtraction
 - Multiplication and division
 - Dealing with overflow
- Floating-point real numbers
 - Representation and operations



Integer Addition

■ Example: $7 + 6$

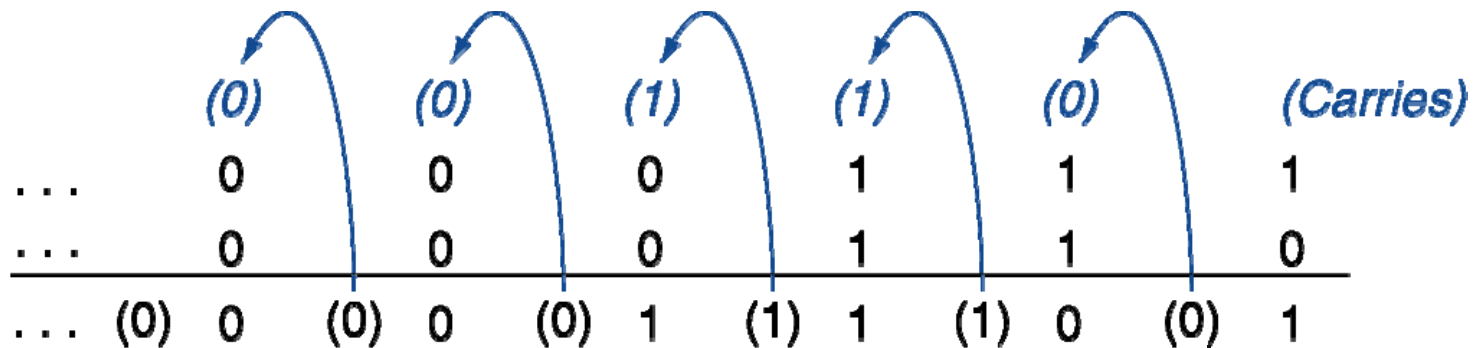

■ Overflow if result out of range

- Adding +ve and -ve operands, no overflow
- Adding two +ve operands
 - Overflow if result sign is 1
- Adding two -ve operands
 - Overflow if result sign is 0



Integer Subtraction

- Add negation of second operand

- Example: $7 - 6 = 7 + (-6)$

+7:	0000 0000 ... 0000 0111
-6:	1111 1111 ... 1111 1010
<hr/>	
+1:	0000 0000 ... 0000 0001

- Overflow if result out of range

- Subtracting two +ve or two -ve operands, no overflow
- Subtracting +ve from -ve operand
 - Overflow if result sign is 0
- Subtracting -ve from +ve operand
 - Overflow if result sign is 1




Dealing with Overflow

- Some languages (e.g., C) ignore overflow
 - Use MIPS addu, addui, subu instructions
- Other languages (e.g., Ada, Fortran) require raising an exception
 - Use MIPS add, addi, sub instructions
 - On overflow, invoke exception handler
 - Save PC in exception program counter (EPC) register
 - Jump to predefined handler address
 - mfc0 (move from coprocessor reg) instruction can retrieve EPC value, to return after corrective action




Arithmetic Logic Unit Design

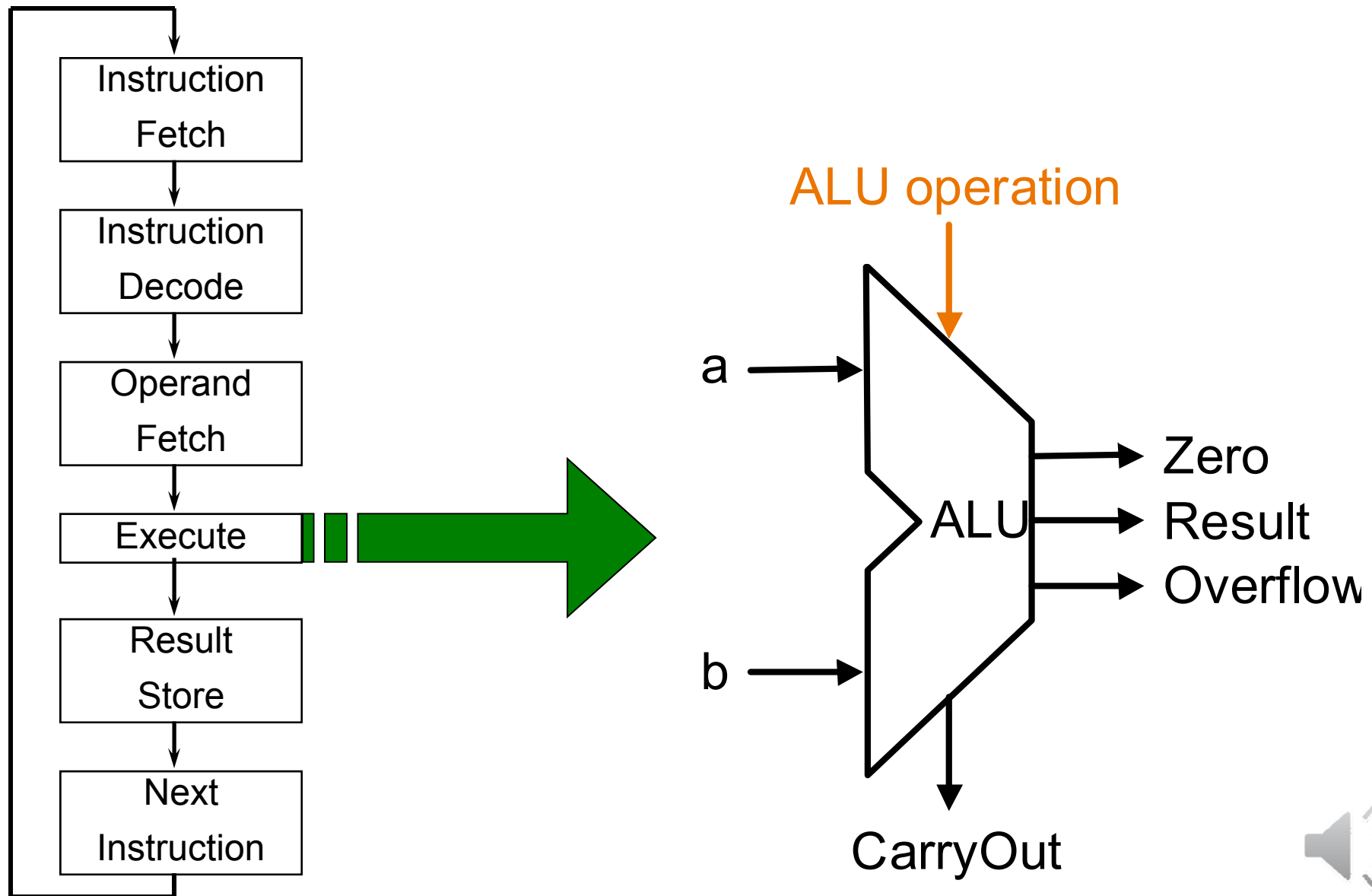


One Bit ALU

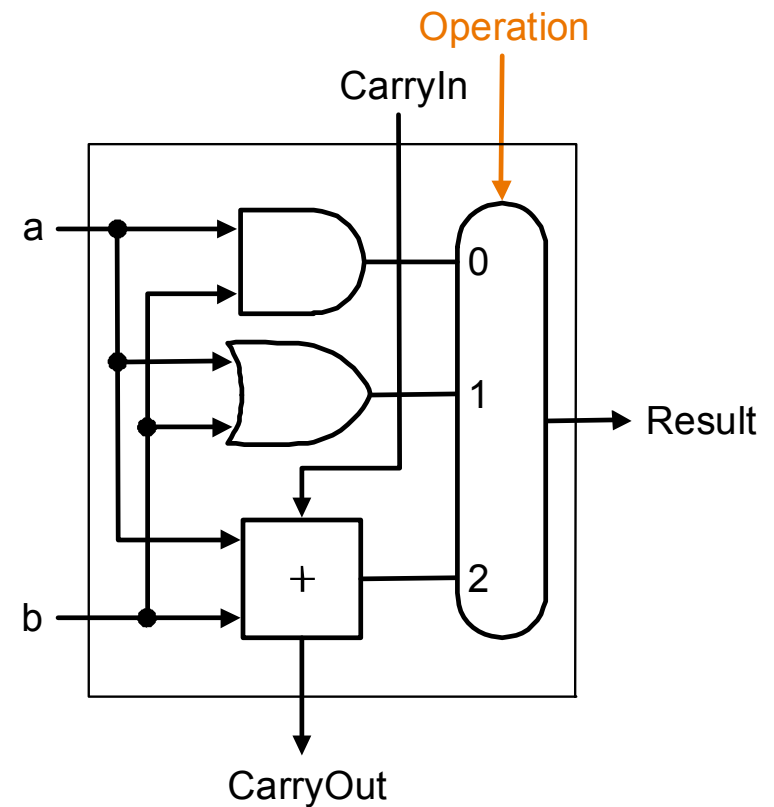- Performs AND, OR, and ADD
 - on 1-bit operands
 - components:
 - AND gate
 - OR gate
 - 1-bit adder
 - Multiplexor



One Bit Full Adder

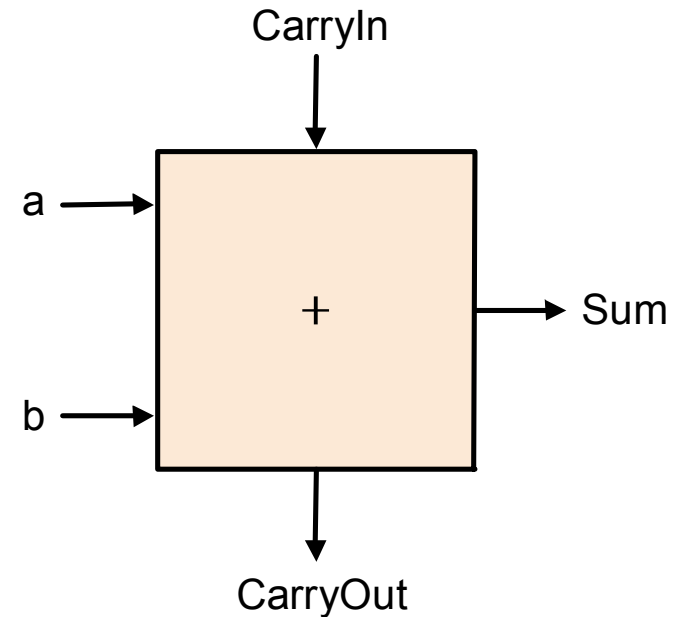- Also known as a (3,2) adder
- Half Adder
 - no CarryIn



Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	0+0+0=00
0	0	1	0	1	0+0+1=01
0	1	0	0	1	0+1+0=01
0	1	1	1	0	0+1+1=10
1	0	0	0	1	1+0+0=01
1	0	1	1	0	1+0+1=10
1	1	0	1	0	1+0+1=10
1	1	1	1	1	1+1+1=11



CarryOut Logic Equation

- $\text{CarryOut} = (!a \ \& \ b \ \& \ \text{CarryIn}) \mid (a \ \& \ !b \ \& \ \text{CarryIn}) \mid (a \ \& \ b \ \& \ !\text{CarryIn}) \mid (a \ \& \ b \ \& \ \text{CarryIn})$
- $\text{CarryOut} = (b \ \& \ \text{CarryIn}) \mid (a \ \& \ \text{CarryIn}) \mid (a \ \& \ b)$

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	0+0+0=00
0	0	1	0	1	0+0+1=01
0	1	0	0	1	0+1+0=01
0	1	1	1	0	0+1+1=10
1	0	0	0	1	1+0+0=01
1	0	1	1	0	1+0+1=10
1	1	0	1	0	1+0+1=10
1	1	1	1	1	1+1+1=11



Sum Logic Equation

- Sum = $(!a \ \& \ !b \ \& \ \text{CarryIn}) \mid (!a \ \& \ b \ \& \ !\text{CarryIn}) \mid (a \ \& \ !b \ \& \ !\text{CarryIn}) \mid (a \ \& \ b \ \& \ \text{CarryIn})$

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	0+0+0=00
0	0	1	0	1	0+0+1=01
0	1	0	0	1	0+1+0=01
0	1	1	1	0	0+1+1=10
1	0	0	0	1	1+0+0=01
1	0	1	1	0	1+0+1=10
1	1	0	1	0	1+0+1=10
1	1	1	1	1	1+1+1=11

