


# Chapter 3

## Arithmetic for Computers




# 32-bit ALU

## ■ Ripple Carry ALU

 

1-bit ALU

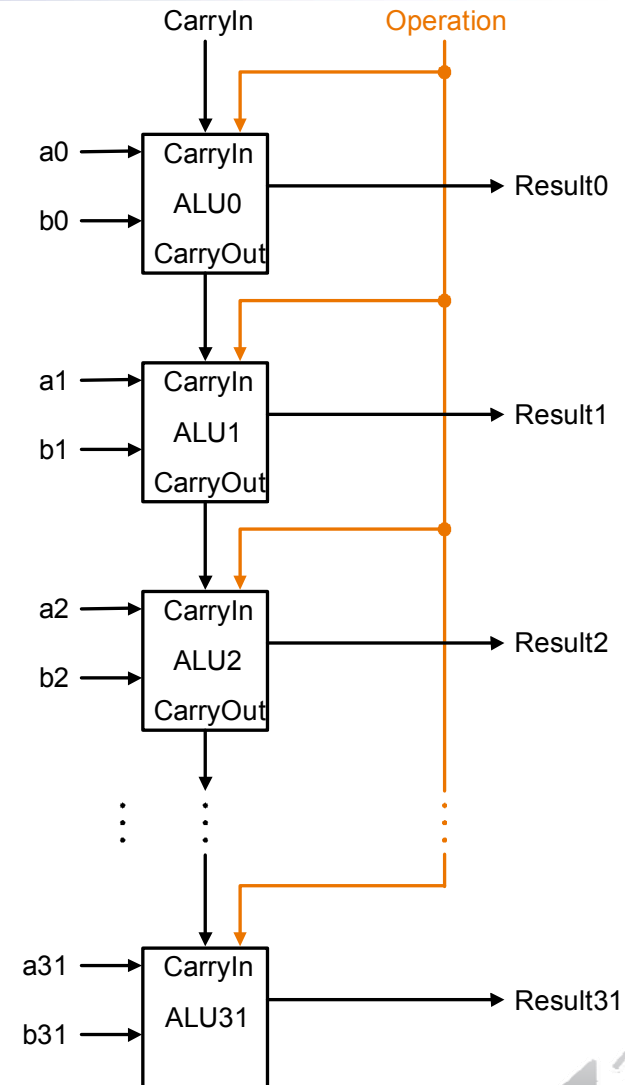


32-bit ALU


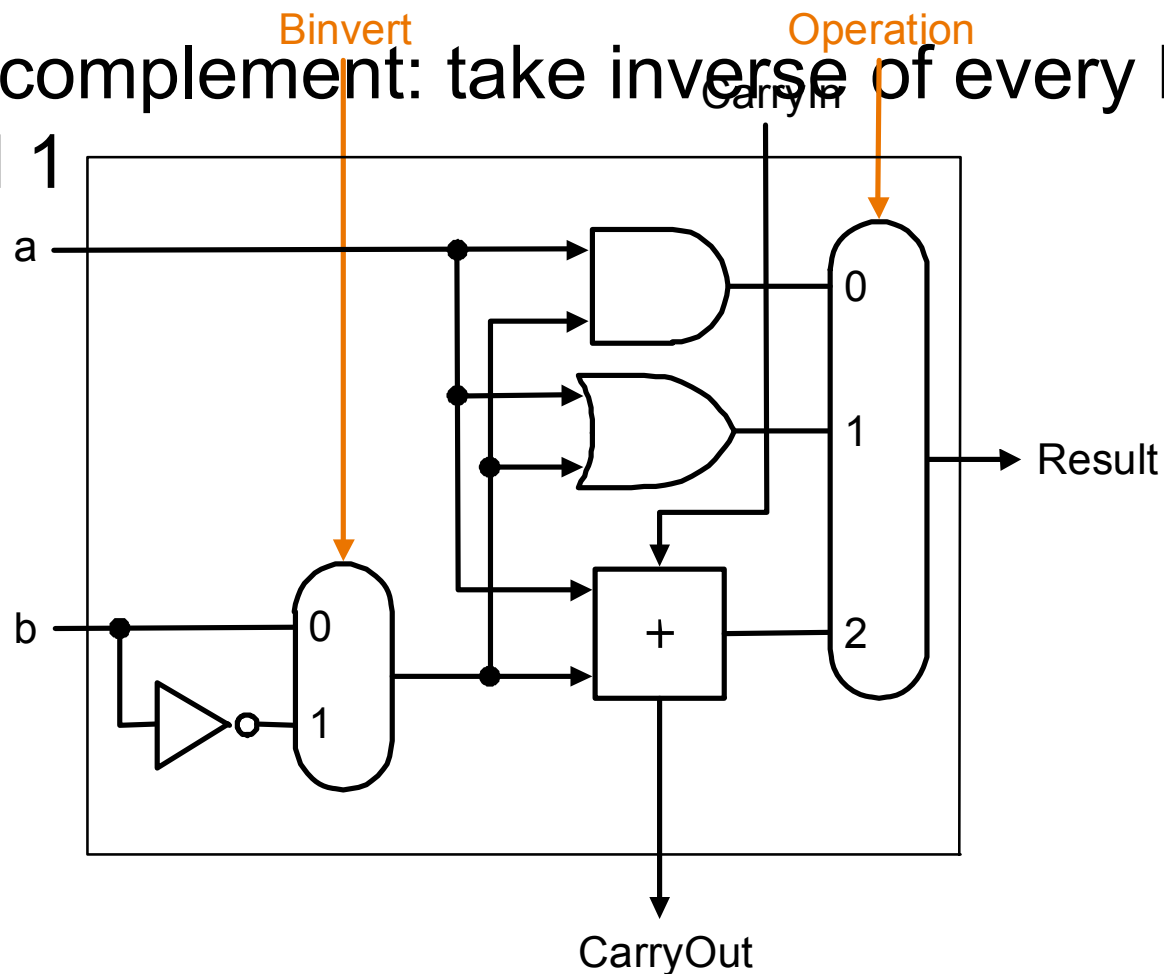
# Subtraction?


- Expand our 1-bit ALU to include an inverter
  - 2's complement: take inverse of every bit and add 1


 
# Overflow

- For N-bit ALU

- $\text{Overflow} = \text{CarryIn}[N-1] \text{ XOR } \text{CarryOut}[N-1]$



Most significant (N-1) bit ALU




# Zero Detection

- Conditional Branches
- One big NOR gate
- $\text{Zero} = (\text{Result}_{N-1} + \text{Result}_{N-2} + \dots + \text{Result}_1 + \text{Result}_0)$
- Any non-zero result will cause zero detection output to be zero



# NOR

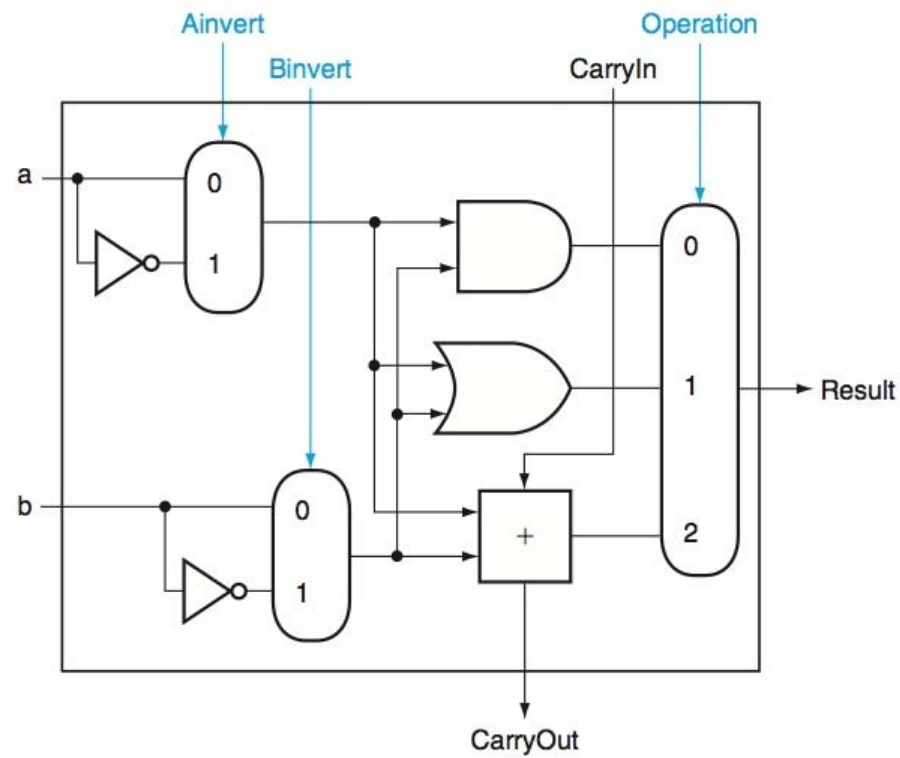


# Set-On-Less-Than (SLT)


- SLT produces a 1 if  $rs < rt$ , and 0 otherwise
  - all but least significant bit will be 0
  - how do we set the least significant bit?
  - can we use subtraction?
    - $rs - rt < 0$
  - set the least significant bit to the sign-bit of  $(rs - rt)$
- New input: LESS
- New output: SET



# SLT Implementation

 

All but MSB

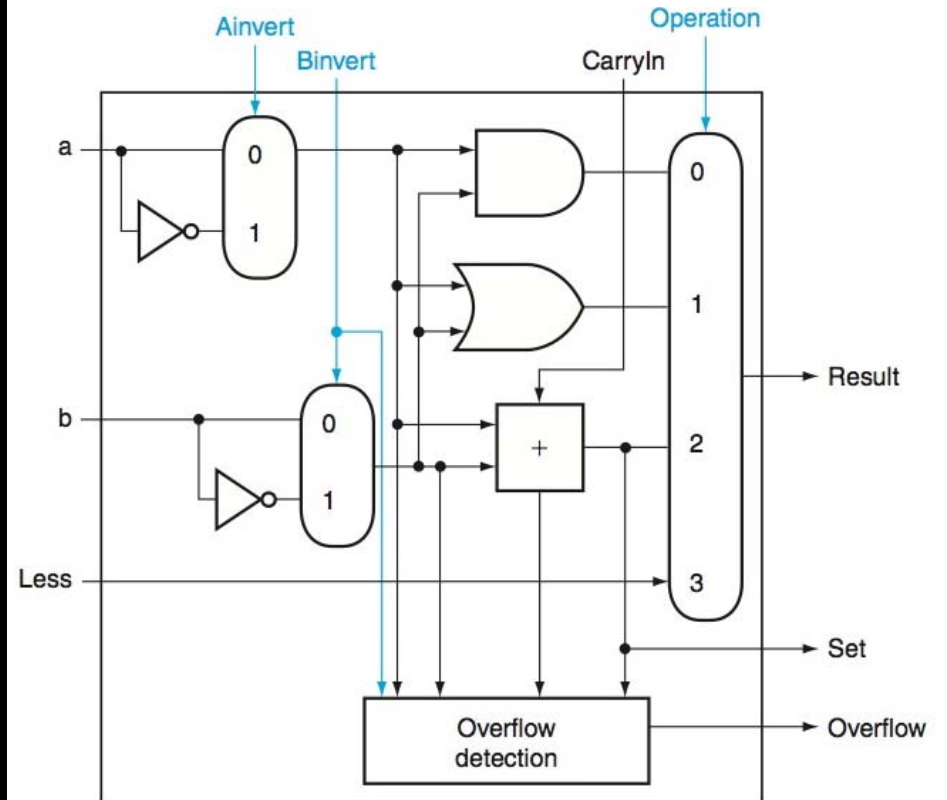


Most Significant Bit




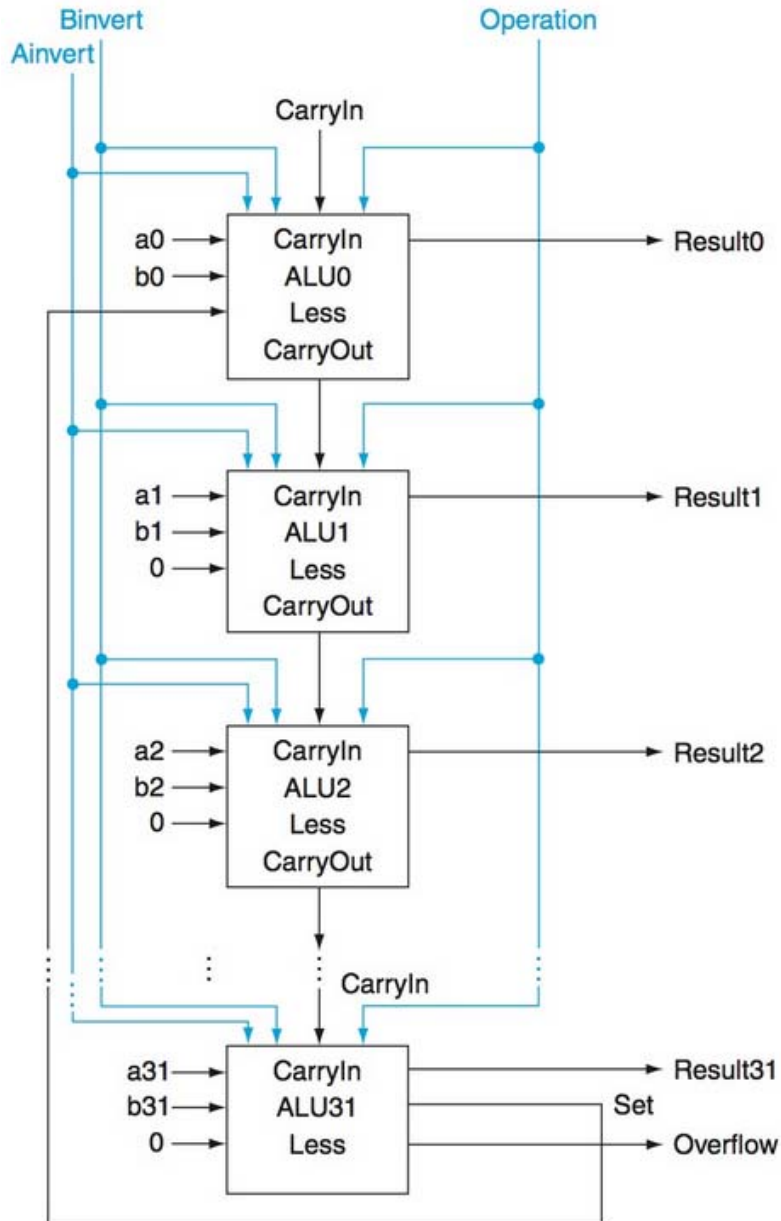
# SLT Implementation

- Set of MSB is connected to Less of LSB!



# Final ALU

- You should feel comfortable identifying what signals accomplish:
  - add
  - sub
  - and
  - or
  - nor
  - slt

